

2026 Digital IC Design

Homework 1: 4-bit Ripple Carry Adder

1. Introduction:

This homework focuses on designing digital modules to implement a 4-bit Ripple Carry Adder (RCA) circuit using **hierarchical design**. You are requested to design a 1-bit Half Adder (HA) module, which performs binary addition of two 1-bit inputs and outputs the sum and carry. The Half Adder is then used to construct a Full Adder (FA), which includes two Half Adders to incorporate the carry-in bit.

The Full Adder is further used to construct a 4-bit Ripple Carry Adder, which computes the sum of two 4-bit unsigned binary numbers along with an input carry. The circuit should be implemented by hierarchical module composition: starting from **Half Adder** → **Full Adder** → **RCA**.

You are encouraged to verify the correctness of each level using comprehensive testbenches. The overall architecture should follow the hierarchical design as shown in the provided diagram.

1.1 1-bit Half Adder

The Half Adder circuit used in this architecture is shown in Figure 1, and its specification and I/O interface are listed in Table I. The Half Adder takes two 1-bit binary inputs and computes a 1-bit sum and a 1-bit carry as outputs.

 


Fig 1. Architecture of the Half Adder

Table I. Specification and I/O interface of Half Adder

Signal Name	I/O	Width	Description
x	I	1	First 1-bit input operand
y	I	1	Second 1-bit input operand
s	O	1	The sum of the input x and y
c	O	1	A carry when both x and y are 1

1.2 1-bit Full Adder

The architecture of the Full Adder module for this homework is shown in Figure 2, and its specification and I/O interface is listed in Table II. The Full Adder module takes three 1-bit binary inputs—two operands and one carry-in—and produces a 1-bit sum and a 1-bit carry-out as outputs.

In this homework, you must construct the Full Adder circuit using your 1-bit Half Adder module in a hierarchical design.

 


Fig 2. Architecture of the Full Adder

Table II. Specification and I/O interface of Full Adder

Signal Name	I/O	Width	Description
x	I	1	First 1-bit input operand
y	I	1	Second 1-bit input operand
c_in	I	1	Carry-in input from the previous adder stage
s	O	1	1-bit sum result of the addition
c_out	O	1	Carry-out to be passed to the next adder stage

1.3 4-bit Ripple Carry Adder

The architecture of the Ripple Carry Adder (RCA) module for this homework is shown in Figure 3, and its specification and I/O interface is listed in Table III. The RCA module takes two 4-bit binary inputs and a 1-bit carry-in, and produces a 4-bit sum along with a 1-bit carry-out as outputs.

In this homework, you must construct the RCA circuit using your previously designed 1-bit Full Adder modules in a hierarchical and cascaded structure.

 


Fig 3. Architecture of the RCA

Table III. Specification and I/O interface of RCA

Signal Name	I/O	Width	Description
x	I	4	First 4-bit input operand
y	I	4	Second 4-bit input operand
c_in	I	1	Carry-in input, typically applied to the least significant bit (LSB)
s	O	4	4-bit sum result of the addition

c_out	O	1	Final carry-out generated from the most significant bit (MSB)
-------	---	---	---

1.4 File Description

File Name	Description
HA.v	The module of 1-bit Half Adder
FA.v	The module of 1-bit Full Adder
RCA.v	The module of 4-bit Ripple Carry Adder
testfixture.sv	Testbench file. This file is not allowed to be modified

2. Scoring:

2.1 1-bit Half Adder [20%]

The result should be generated correctly, and you will get the following message in ModelSim simulation.

```

-
# === Testing Half Adder ===
# PASS: #0 data is correct
# PASS: #1 data is correct
# PASS: #2 data is correct
# PASS: #3 data is correct
# PASS: #4 data is correct
# PASS: #5 data is correct
# PASS: #6 data is correct
# PASS: #7 data is correct
# >>> [HA] TEST PASSED

```

Fig. 4 Simulation result for Half Adder

2.2 1-bit Full Adder [30%]

The result should be generated correctly, and you will get the following message in ModelSim simulation. **Please construct the Full Adder circuit with your Half Adder modules. Otherwise, you can just get half of the points.**

```
# === Testing Full Adder ===  
# PASS: #0 data is correct  
# PASS: #1 data is correct  
# PASS: #2 data is correct  
# PASS: #3 data is correct  
# PASS: #4 data is correct  
# PASS: #5 data is correct  
# PASS: #6 data is correct  
# PASS: #7 data is correct  
# >>> [FA] TEST PASSED
```

Fig. 5 Simulation result for Full Adder

2.3 4-bit Ripple Carry Adder [50%]

The result should be generated correctly, and you will get the following message in ModelSim simulation. **Please construct the Ripple Carry Adder circuit with your Full Adder modules. Otherwise, you can just get half of the points.**

```
# === Testing Ripple Carry Adder ===  
# PASS: #0 data is correct  
# PASS: #1 data is correct  
# PASS: #2 data is correct  
# PASS: #3 data is correct  
# PASS: #4 data is correct  
# PASS: #5 data is correct  
# PASS: #6 data is correct  
# PASS: #7 data is correct  
# PASS: #8 data is correct  
# PASS: #9 data is correct  
# >>> [RCA] TEST PASSED
```

Fig. 6 Simulation result for RCA


3. Submission

3.1. File Submission

You should classify your files into two directories and compress them to .zip format. The naming rule is StudentID.zip. **If your file is not named according to the naming rule, you will lose five points.**

	RTL
*.v	All of your Verilog RTL code
	Documentary
Report.pdf	The report file of your design (in pdf).

Fig. 7 File hierarchy

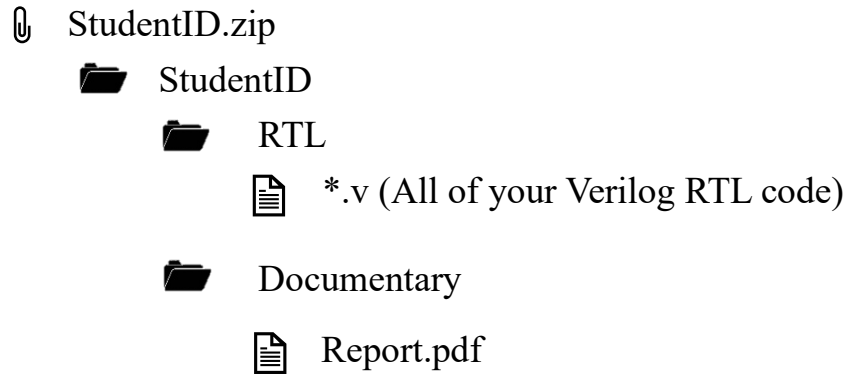

3.2. Report File

Please follow the spec of report. You are asked to describe how the circuit is designed as detailed as possible.

3.3. Notes

- Please submit your .zip file to folder HW1 in moodle.
Deadline: 2025/10/05 23:55
- Late submission will only be accepted within a week and will result in a penalty of 5 points per day.
- TA email: p76135038@gs.ncku.edu.tw