

2026 Digital IC Design

Homework 2: Modular Multiplier

1. Introduction:

This homework aims to design a resource-efficient modular multiplier for two 23-bit inputs under a fixed modulus $Q=8380417$. The circuit avoids costly division by using constant multipliers and bitwise operations. You will implement a combinational module **Mul_Mod** that outputs $Z=(A \times B) \bmod Q$, suitable for cryptographic applications like Kyber or Dilithium.

1.1 23-bit Dual-Input Mul_Mod

The logic diagram of the Mul_Mod circuit is shown in Fig. 1, and its I/O specification is listed in Table I. The module performs modular multiplication between two 23-bit unsigned inputs A and B, producing a 24-bit result $Z = (A \times B) \bmod 8380417$. The design uses partial multipliers, shifts, and constant multiplications to efficiently implement the operation without full-width multiplication or division. **In this homework, you must design the adder module in Mul_Mod using Ripple Carry Adder (RCA) in homework 1.**

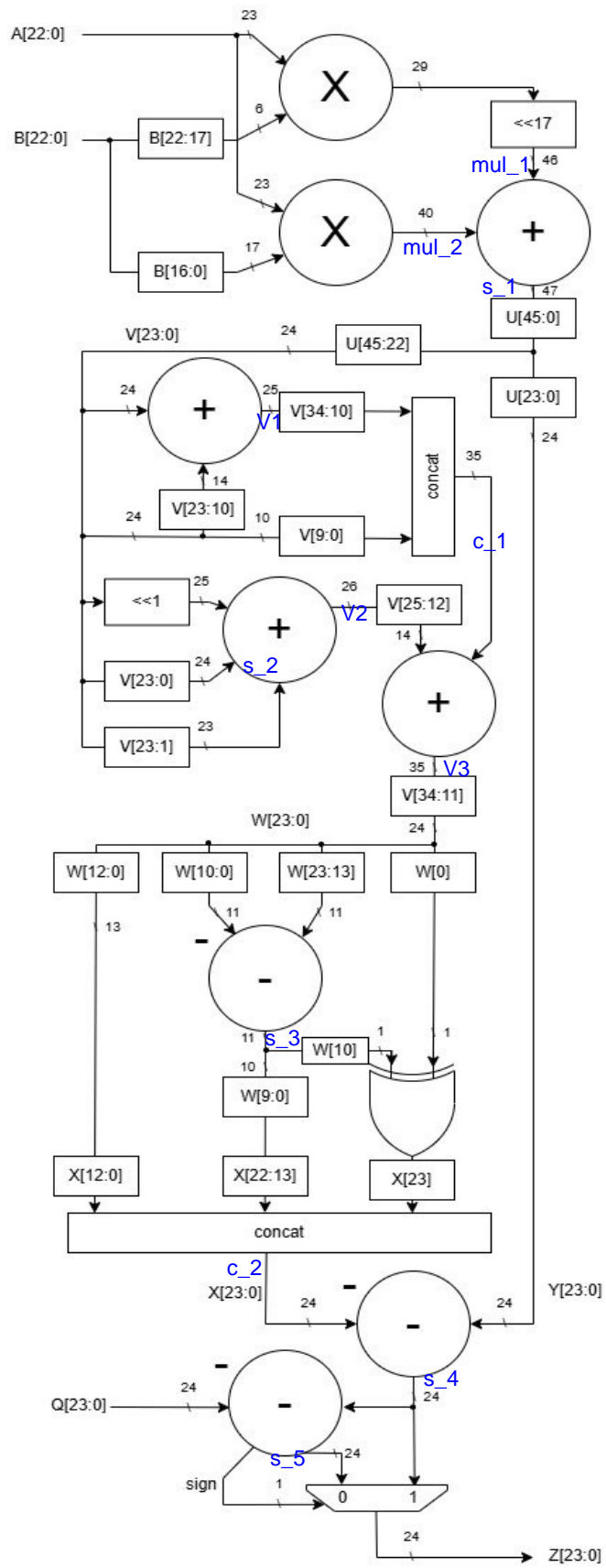


Fig. 1 Logic diagram of the Mul_Mod.

Table I. Specification and I/O interface of Mul_Mod

| Signal Name | I/O | Width | Description |
|-------------|-----|-------|----------------------------------|
| A | I | 23 | First 24-bit input operand |
| B | I | 23 | Second 24-bit input operand |
| Z | O | 24 | The result of modular multiplier |

1.2 File Description

| File Name | Description |
|----------------|---|
| Mul_Mod.v | The module of 23-bit Modular Multiplier. |
| testfixture.sv | Testbench file. This file is not allowed to be modified. |
| golden.dat | Test and golden data file for Mul_Mod. |

2. Scoring:

2.1 23-bit Dual-Input Mul_Mod [100%]

The result should be generated correctly, and you will get the following message in ModelSim simulation.

```

Begin testing full_modular_multiplier
Test 1: A=2125996, B=2235065 => Z=908655 [PASS]
Test 2: A=4874107, B=2121067 => Z=7210127 [PASS]
Test 3: A=2817966, B=408065 => Z=2757552 [PASS]
Test 4: A=7247692, B=3401214 => Z=5175090 [PASS]
Test 5: A=5295674, B=1532595 => Z=8085376 [PASS]
Test 6: A=2778196, B=7775964 => Z=4192923 [PASS]
Test 7: A=6849659, B=3769492 => Z=5242908 [PASS]
Test 8: A=8078964, B=3142723 => Z=6104497 [PASS]
Test 9: A=5499700, B=4593447 => Z=6168991 [PASS]
Test 10: A=7266683, B=8328230 => Z=4244363 [PASS]
=== TEST SUMMARY ===
Total tests: 10
Passed      : 10
Failed      : 0
=====

```

Fig. 2 Simulation result for Mul_Mod


3. Submission

3.1. File Submission

You should classify your files into two directories and compress them to .zip format. The naming rule is StudentID.zip. **If your file is not named according to the naming rule, you will lose five points.**

| | |
|------------|--|
| | RTL |
| *.v | All of your Verilog RTL code |
| | Documentary |
| Report.pdf | The report file of your design (in pdf). |

Fig. 3 File hierarchy

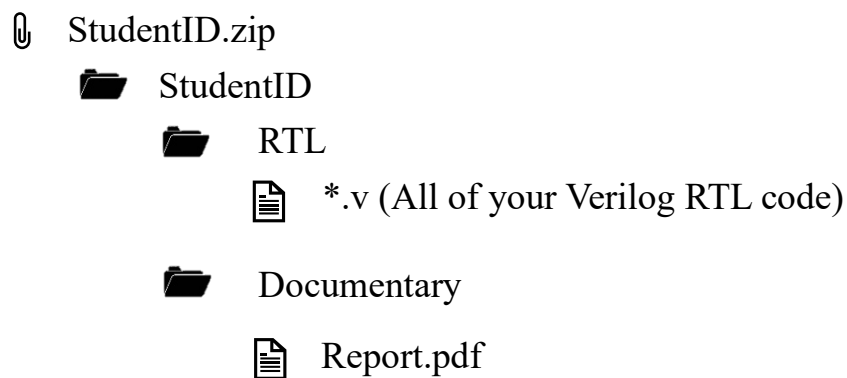

3.2. Report File

Please follow the spec of report. You are asked to describe how the circuit is designed as detailed as possible.

3.3. Notes

- Please submit your .zip file to folder HW2 in moodle.
Deadline: 2025/10/12 23:55
- Late submission will only be accepted within a week and will result in a penalty of 5 points per day.
- TA email: p76134799@gs.ncku.edu.tw